

controlled rectifiers (unit 3)

for a single phase half bridge converter having highly inductive load derive the following.

- 1) fourier series of supply current.
- 2) fundamental component of supply current.
- 3) RMS value of supply current.

1) Fourier series

$$i_s(\omega t) = I_{s(av)} + \sum_{n=1}^{\infty} C_n \sin(n\omega t + \phi_n)$$

$$\text{where } C_n = \sqrt{a_n^2 + b_n^2}, \quad \phi_n = \tan^{-1}\left(\frac{a_n}{b_n}\right)$$

$$\text{— Here, } a_n = \frac{2}{T} \int_0^T i_s(\omega t) \cos n\omega t \, d\omega t$$

$$= \frac{2}{2\pi} \int_0^{2\pi} i_s(\omega t) \cos n\omega t \, d\omega t \quad \text{--- (1)}$$

from supply current waveform,

$$a_n = \frac{2}{2\pi} \left[\int_{\alpha}^{\pi} I_{o(av)} \cos n\omega t \, d\omega t + \int_{\pi+\alpha}^{2\pi} (-I_{o(av)}) \cos n\omega t \, d\omega t \right]$$
$$= \frac{I_{o(av)}}{\pi} \left[\int_{\alpha}^{\pi} \cos n\omega t \, d\omega t - \int_{\pi+\alpha}^{2\pi} \cos n\omega t \, d\omega t \right]$$

$$= \frac{-I_{oav}}{n\pi} \sin n\alpha (1 - \cos n\pi)$$

$$a_n = \begin{cases} \frac{-2 I_{oav}}{n\pi} \sin n\alpha & \text{for } n = 1, 3, 5 \\ 0 & \text{for } n = 2, 4, 6 \end{cases}$$

Q Shows that 'a_n = 0' for even harmonics of supply current.

$$a_n = \frac{2}{T} \int_0^T i_s(\omega t) \sin n\omega t d\omega t \quad (\text{Put } T = 2\pi)$$

$$= \frac{2}{2\pi} \left[\int_{\alpha}^{\pi} I_{oav} \sin n\omega t d\omega t + \int_{\pi+\alpha}^{2\pi} (-I_{oav}) \sin n\omega t d\omega t \right]$$

$$= \frac{I_{oav}}{\pi} \left[\int_{\alpha}^{\pi} \sin n\omega t d\omega t - \int_{\pi+\alpha}^{2\pi} \sin n\omega t d\omega t \right]$$

$$= \frac{I_{oav}}{n\pi} (1 + \cos n\alpha) (1 - \cos n\pi)$$

$$b_n = \begin{cases} \frac{2 I_{oav}}{n\pi} (1 + \cos n\alpha) & \text{for } n = 1, 3, 5 \\ 0 & \text{for } n = 2, 4, 6 \end{cases}$$

$$\text{now } C_n = \sqrt{a_n^2 + b_n^2}$$

$$= \left\{ \left[-\frac{2I_0(\omega)}{n\pi} \sin n\alpha \right]^2 + \left[\frac{2I_0}{n\pi} (1 + \cos n\alpha) \right]^2 \right\}$$

$$C_n = \frac{4 I_0(\omega) \cos(n\alpha)}{n\pi} \text{ for } n=1, 3, 5$$

②.

$$\text{now } \phi_n = \tan^{-1} \left(\frac{a_n}{b_n} \right)$$

$$= \tan^{-1} \left[\frac{-\frac{2I_0}{n\pi} \sin n\alpha}{\frac{2I_0}{n\pi} (1 + \cos n\alpha)} \right]$$

$$\phi_n = -\tan^{-1} \left(\tan \frac{n\alpha}{2} \right)$$

$$\boxed{\phi_n = -\frac{n\alpha}{2}} \quad \text{--- (3)}$$

$$\text{now } I_s(\omega) = \frac{1}{T} \int_0^T i_s(\omega t) d\omega t \quad (\text{put } T=2\pi)$$

$$= \frac{1}{2\pi} \left\{ \int_0^{2\pi} I_0(\omega) d\omega t + \int_{\pi+\alpha}^{2\pi} -I_0 \omega d\omega t \right\}$$

$$= \frac{I_0(\alpha\omega)}{2\pi} \left[\int_{\alpha}^{\pi} d\omega t - \int_{\pi+\alpha}^{2\pi} d\omega t \right]$$

$$I_1(\omega t) = \frac{I_0(\alpha\omega)}{2\pi} \left\{ (\omega t)_{\alpha}^{\pi} - (\omega t)_{\pi+\alpha}^{2\pi} \right\}$$

$$= \frac{I_0(\alpha\omega)}{2\pi} \left\{ \pi + \alpha - 2\pi - \pi - \alpha \right\}$$

hence fourier series can be written as

$$I_s(\omega t) = \sum_{n=1,3,5}^{\infty} \frac{4I_0(\alpha\omega)}{n\pi} \cos\left(\frac{n\alpha}{2}\right) \sin\left(n\omega t - \frac{n\alpha}{2}\right)$$

④

① fundamental component of supply current:

$$I_{s1} \Rightarrow \frac{C_1}{\sqrt{2}}, \quad C_1 = \frac{4I_0(\alpha\omega) \cos \frac{\alpha}{2}}{\pi} \text{ with } n=1$$

$$I_{s1} = \frac{4I_0(\alpha\omega) \cos \frac{\alpha}{2}}{\pi} \times \frac{1}{\sqrt{2}}$$

$$I_{s1} = \frac{2\sqrt{2} I_0(\alpha\omega) \cos \frac{\alpha}{2}}{\pi}$$

© R.M.S value of I_s

$$I_{s(rms)} = \left[\frac{1}{T} \int_0^T i_s^2(\omega t) d\omega t \right]^{1/2}$$

$$= \left\{ \frac{1}{2\pi} \left[\int_{\alpha}^{\pi} I_{o(av)}^2 d\omega t + \int_{\pi+\alpha}^{2\pi} \left(-\frac{I_{o(av)}}{\alpha(\omega t)} \right)^2 d\omega t \right] \right\}^{1/2}$$

$$= \left[\frac{I_{o(av)}^2}{2\pi} \left(\int_{\alpha}^{\pi} d\omega t + \int_{\pi+\alpha}^{2\pi} d\omega t \right) \right]^{1/2}$$

$$I_{s(rms)} = \sqrt{\frac{\pi - \alpha}{\pi}}$$