
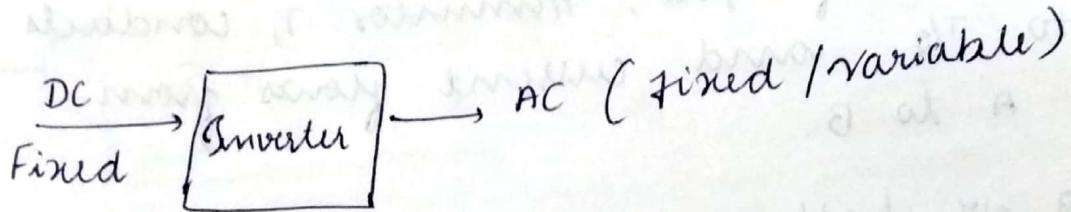
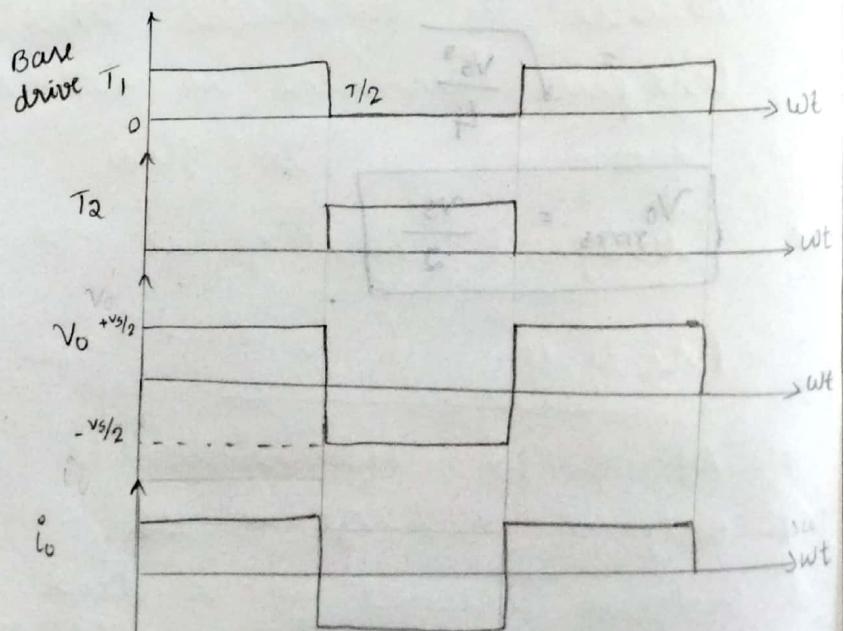


Unit - 05Inverter

- * Inverter → DC to AC converter
- * The output voltage could be fixed or variable at a fixed or variable frequency
- * For fixed output voltage → gain of an inverter is variable.
- * For variable output voltage → gain is constant.
- * The inverter gain = $\frac{\text{AC output voltage}}{\text{DC input voltage}}$.

- * Inverter
 - Half bridge inverter
 - Full bridge inverter.

1. Half bridge inverter :

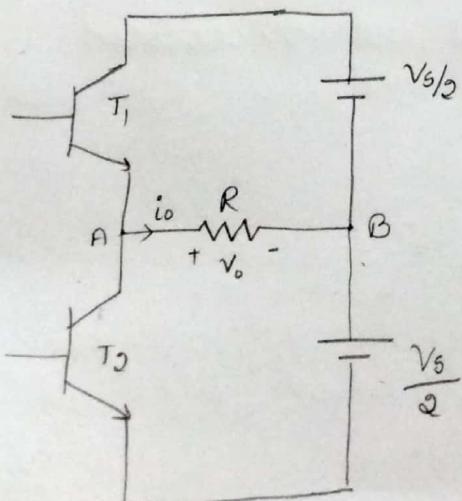

- * Half bridge inverter consist of two transistors T_1 and T_2 which are used as switch.
 - * During +ve half cycle, transistor T_1 conducts from 0 to $T/2$ and current flows from point A to B.
 - * During -ve half cycle, transistor T_2 conducts from $T/2$ to T and current flows from B to A.
 - * Since the load is resistive, the o/p current waveform is same as voltage waveform.
 - * The output $v_{tg} = \pm \frac{v_s}{2}$
- The rms value of an output voltage is given by

$$V_{o,\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v_o^2 dt}$$



$$= \sqrt{\frac{1}{T} \int_0^T \left[\frac{v_s}{2} \right]^2 dt}$$

$$= \sqrt{\frac{1}{T} \times \frac{v_s^2}{4} \int_0^T dt} = \sqrt{\frac{v_s^2}{4T} [T - 0]}$$

$$= \sqrt{\frac{v_s^2}{4}}$$

$$\boxed{V_{o,\text{rms}} = \frac{v_s}{2}}$$

Half bridge inverter with RL load

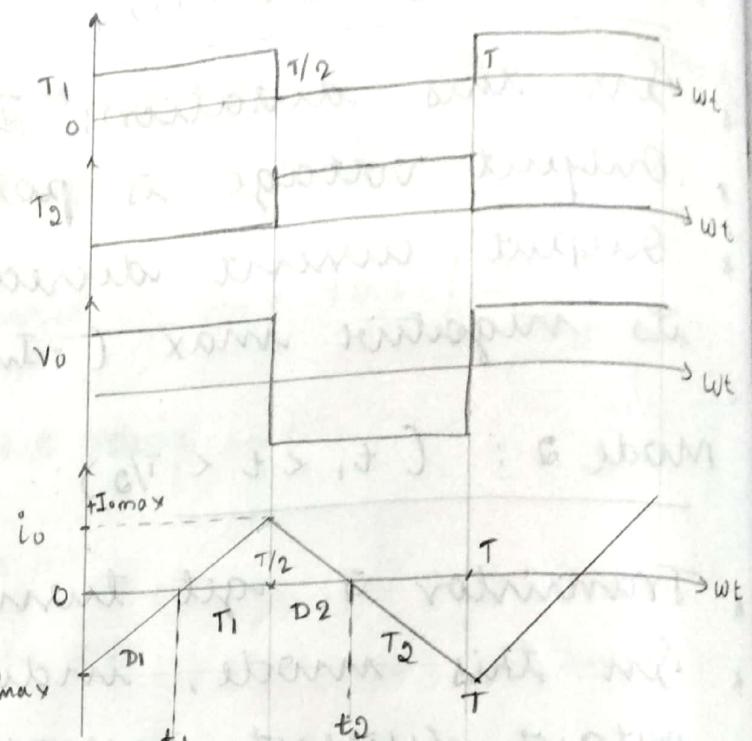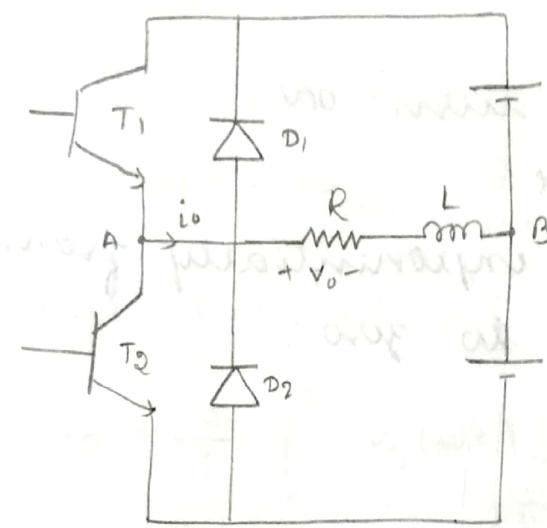

- * A half bridge inverter with RL load consisting of two transistors and 2 feedback diodes.
- * The load RL is connected between point A and B.
- * Mode 1: ($t_1 < t < T/2$): (at $t = 0 \rightarrow \omega$)
- * At $t=t_1$, transistor T_1 gets turn on.

Operation:

Mode 1: ($0 < t < t_1$):

- In this duration, T_1 is turn on.
- Output voltage is positive.
- Output current decreases exponentially from its negative max ($-I_{max}$) to zero.

Mode 2: ($t_1 < t < T_2$):

- Transistor T_1 gets turn on at $t = t_1$.
- In this mode, inductor stores energy and output current increases exponentially from zero to $+I_{max}$.
- The output voltage is +ve and $V_o = V_s/2$.
- At $t = T_2$, output current reaches to its max value and T_1 gets turn OFF.

Mode 3: ($T_2 < t < t_3$):

- Inductor release its energy through D_2 .
- Diode D_2 conduct this time.
- Output current is +ve but it decreases from $+I_{max}$ to zero.
- Output voltage is -ve.

Mode 4: ($t_3 < t < T$):

- At $t = t_3$, transistor T_2 gets turn on.
- Output voltage is -ve.
- Output current is -ve but it increases exponential from 0 to its negative max value.

Obtain the fourier series for the output voltage waveform for half bridge inverter:

The general expression for fourier series is given by

$$v_o(wt) = V_o \text{avg} + \sum_{i=1}^{\infty} C_n \sin(nwt + \phi_n)$$

where $C_n = \sqrt{a_n^2 + b_n^2}$ and $\phi_n = \tan^{-1}\left[\frac{a_n}{b_n}\right]$

$$a_n = \frac{2}{T} \int_0^T v_i(wt) \cos nwt \cdot dwt$$

$$T_1 = \frac{V_s}{2} \rightarrow 0 \text{ to } \pi$$

$$T_2 = -\frac{V_s}{2} \rightarrow \pi \text{ to } 2\pi$$

$$a_n = \frac{2}{2\pi} \int_0^{\pi} \frac{V_s}{2} \cos nwt \cdot dwt$$

$$= \frac{V_s}{2\pi} \left[\sin nwt \right]_0^{\pi} = \frac{V_s}{2\pi} [0 - 0]$$

$$\boxed{a_n = 0} \rightarrow \text{for all values of } n.$$

$$b_n = \frac{2}{T} \int_0^T v_o(wt) \sin nwt \cdot dwt$$

$$= \frac{2}{2\pi} \int_0^{\pi} \frac{V_s}{2} \sin nwt \cdot dwt$$

$$= \frac{V_s}{2\pi} \left[-\cos nwt \right]_0^{\pi}$$

$$= \frac{V_s}{2\pi} [-\cos n\pi + \cos 0]$$

$$\boxed{b_n = \frac{V_s}{n\pi} [1 - \cos n\pi]} \rightarrow \text{general eqn.}$$

Here, $\cos n\pi = \begin{cases} 1 & \text{for } n=0, 4, 8, \dots \\ -1 & \text{for } n=1, 3, 5, \dots \end{cases}$

Hence $b_n = \begin{cases} \frac{2V_s}{n\pi} & \text{for odd values} \\ 0 & \text{for even value of } n \end{cases}$

$$\therefore C_n = \sqrt{a_n^2 + b_n^2} = b_n = \frac{2V_s}{n\pi}$$

$$\phi_n = \tan^{-1}\left(\frac{a_n}{b_n}\right) = \underline{\underline{0}}$$

The waveform of half bridge inverter has symmetric +ve and -ve half cycle, hence avg output voltage is zero.

$$v_o(wt) = V_o \text{avg} + \sum_{n=1}^{\infty} C_n \sin(nwt + \phi_n)$$

$$v_o(wt) = \sum_{n=1, 3, 5}^{\infty} \frac{2V_s}{n\pi} \sin nwt.$$

The output voltage contains only odd harmonics.

To obtain the rms value of fundamental component by considering the Fourier series equation of half bridge inverter, for fundamental component of output voltage can be written as.

$$v_o(wt) = \frac{2V_s}{\pi} \sin wt \quad (\text{for } n=1)$$

It has same frequency as that of square wave and peak value of fundamental component is given by $C_1 = \frac{2V_s}{\pi}$

and rms value of fundamental component is given by

$$V_{1\text{ rms}} = \frac{C_1}{\sqrt{2}}$$

$$V_{1\text{ rms}} = \frac{\frac{2V_s}{\pi}}{\sqrt{2}} = \frac{2V_s}{\sqrt{2}\pi} = \frac{\sqrt{2}V_s}{\pi} = 0.45 V_s$$

Similarly,

Rms values of other harmonics can be calculated

by $V_{n\text{ rms}} = \frac{2V_s}{\sqrt{2n}\pi} = \frac{0.45 V_s}{n}$

14/01/23

Q) The single phase half bridge inverter has the DC input of 48V and the load resistance is 48Ω. Determine,

- rms value of o/p voltage
- rms value of fundamental component ($n=1$)

$$\rightarrow V_{1\text{ rms}} = 0.45 V_s = 0.45 \times 48 = 21.6 \text{ V}$$

$$\cancel{V_{1\text{ rms}}} = \underline{0.45 V_s}$$

$$V_{o\text{ rms}} = \frac{V_s}{2} = \frac{48}{2} = 24 \text{ V}$$

(Q) value of natural frequency of system will be

Performance parameters of inverter

of generated-
Small wave

1. Harmonic factor of n^{th} harmonic (HF_n):

It is defined as the ratio of rms value of n^{th} harmonic to rms value of fundamental component.

$$\text{HF}_n = \frac{v_n}{v_1} \quad \text{where } v_n = \text{rms value of } n^{\text{th}} \text{ harmonic}$$

$$v_1 = \text{rms value of fundamental component}$$

2. Total harmonic distortion (THD):

It is the ratio of rms values of all the harmonics to rms value of fundamental component

$$\text{THD} = \left[\sum_{n=1,2,3}^{\infty} v_n^2 \right]^{1/2} / v_1$$

- * The total harmonic distortion indicate, the distortion in the waveform
- * It is the measure of closeness of the waveform to sine wave.

3. Distortion factor (DF):

It is defined as the measure of harmonic distortion that remain in the particular w/f after filtering. Due to filtering higher order harmonics are eliminated.

The DF of n^{th} harmonic component is given by

$$\text{DF} = \frac{1}{v_1} \left[\sum_{n=1,2,3}^{\infty} \left(\frac{v_n}{n^2} \right)^2 \right]^{1/2}, \quad \text{DF}_n = \frac{v_n}{v_1 n^2} \text{ for } n > 1$$

4. Lower order harmonic:

It is the harmonic component which has the nearest frequency to the fundamental and its amplitude within 3% of the fundamental component.

Lower order harmonic should have max. possible frequency so that the harmonic distortion is less.

Problems:

- 1) The single phase HB inverter has DC input of 70V and the load resistance is 6.4Ω. Calculate rms o/p voltage, rms values of fundamental component and THD.

$$\rightarrow * V_{o\text{rms}} = \frac{V_s}{2} = \frac{70}{2} = 35V$$

$$* \text{THD} = \frac{(V_{\text{harmonic}})}{V_1}^{1/2}$$

$$V_{\text{harmonic}} = \frac{V_{o\text{rms}}^2 - V_1^2}{V_1^2}$$

$$\text{THD} = \frac{(V_{o\text{rms}}^2 - V_1^2)^{1/2}}{V_1}$$

$$* V_1 = 0.45 \times V_s$$

$$V_1 = 0.45 \times 70$$

$$V_1 = 31.5V$$

$$\text{THD} = \frac{(35^2 - 31.5^2)^{1/2}}{31.5}$$

$$\text{THD} = 0.4843$$

$$\boxed{\text{THD} = 48.43\%}$$

Q) DC input voltage is 36V, resistance = 1.2Ω
Calculate THD.


$$\rightarrow V_{0\text{ rms}} = \frac{V_s}{2} = \frac{36}{2} = \underline{\underline{18V}}$$

$$V_{1\text{ rms}} = 0.45 \times 36 = \underline{\underline{16.2V}}$$

$$\text{THD} = \frac{(V_{0\text{ rms}}^2 - V_1^2)^{1/2}}{V_1} = \frac{(18^2 - 16.2^2)^{1/2}}{16.2}$$

$$\boxed{\text{THD} = 48.43\%}$$


Full bridge inverter :

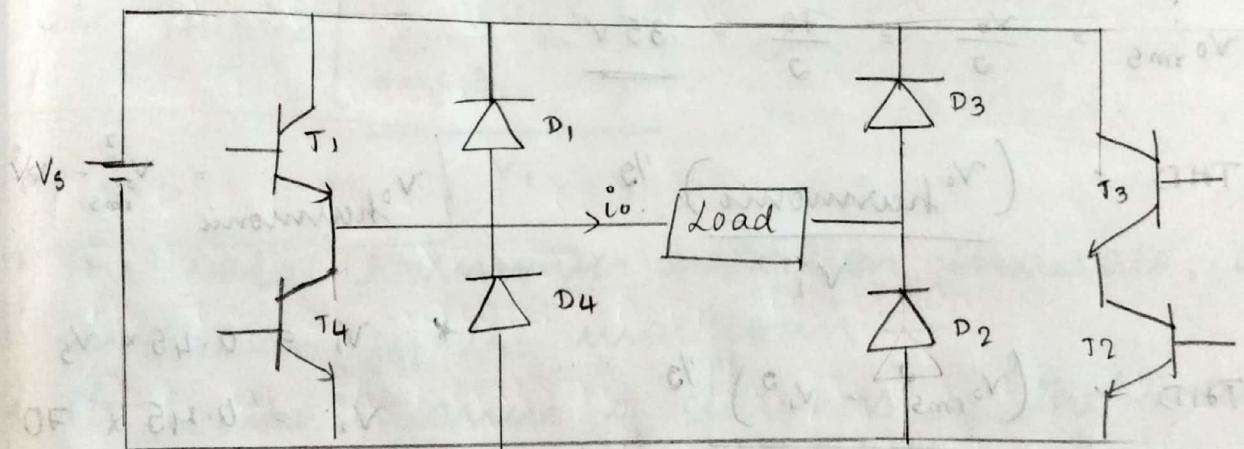

$$V_{0\text{ rms}} = \underline{\underline{18V}}$$

- * A single phase full bridge inverter consist of 4 transistor and 4 feedback diodes.
- * Load can be R load or RL load.
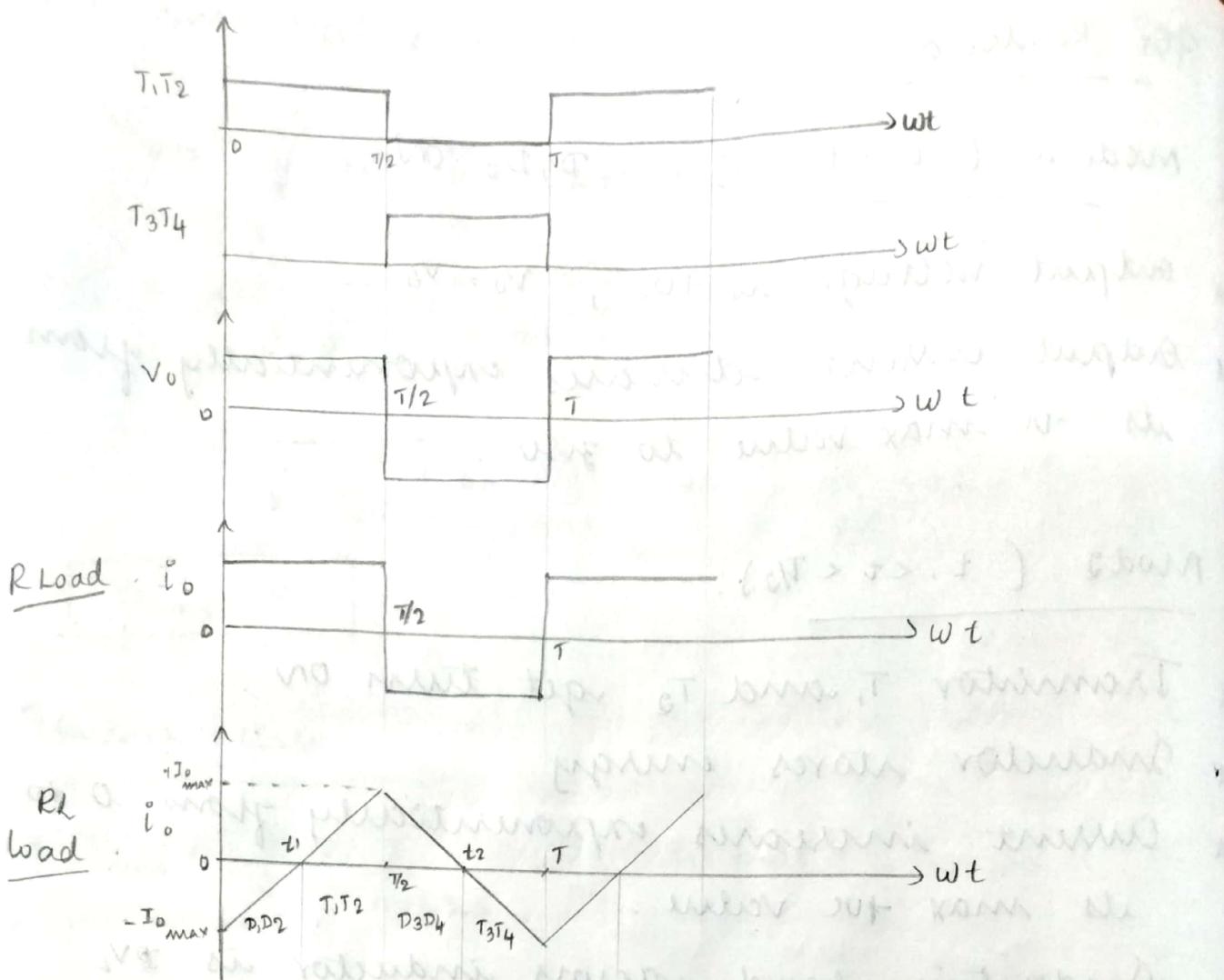
$$\boxed{V_{0\text{ rms}} = \underline{\underline{18V}}}$$



* At $t = 0$

For R load:

- * During 0 to $T/2$, transistors T_1 and T_2 get turn on.
- * The output voltage is $v_o = v_s$.
- * The output current across the load is $+ve$.
- * During $(T/2$ to $T)$:
 - Transistor T_3 and T_4 get turn on ($T_1 T_2$ -OFF).
 - The current flow across the load is $-ve$.
 - The output voltage is also $-ve$, $v_o = -v_s$.

Output voltage $v_o = \underline{\underline{+v_s}}$

FOR RL load:

- * Mode 1 ($0 < t < t_1$): D_1, D_2 ON.
Output voltage is +ve, $V_o = V_S$.
- * Output current decreases exponentially from its +ve max value to zero.

Mode 2 ($t_1 < t < T/2$):

- * Transistor T_1 and T_2 get turn on.
- * Inductor stores energy
- * Current increases exponentially from 0 to its max +ve value.
- * Inductive load across inductor is $-V_L$
- * Output voltage is +ve, $V_o = V_S$.

Mode 3 ($T/2 < t < t_2$)

- * At $t = T/2$, diode D_3, D_4 turn on
- * Due to the energy dissipated by inductor, output current decreases exponentially from $+I_{max}$ to zero.
- * The output voltage is -ve.

Mode 4 ($t_2 < t < T$):

- * Thyristor T_3 and T_4 get turn on
- * Inductor stores energy in reverse direction
- * Output v_{tg} is -ve ($V_o = -V_S$)
- * Current increases from 0 to its -ve max value.

The rms value of output voltage is given by

$$\begin{aligned}
 V_o_{rms} &= \sqrt{\frac{1}{T} \int_0^{2\pi} v_o^2(wt) \cdot dwt} \\
 &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_s^2 \cos^2 wt \cdot dwt} \\
 &= \sqrt{\frac{v_s^2}{2\pi} [2\pi - 0]} = \sqrt{\frac{v_s^2}{2\pi} \times 2\pi} \\
 V_o_{rms} &= v_s
 \end{aligned}$$

Fourier series:

$$V_o_{rms} = \frac{v_s}{2} = \sum_{n=1,3,5}^{\infty} \frac{4v_s}{n\pi} \sin nwt$$

$$V_{1rms} = 0.9v_s$$

$$V_{n rms} = \frac{0.9v_s}{n}$$

$$c_n = \sqrt{a_n^2 + b_n^2} = \frac{4v_s}{n\pi}$$

$$\phi_n = \tan^{-1} \left(\frac{a_n}{b_n} \right) = 0$$

→ Fundamental component.

$$c_1 = \frac{4v_s}{\pi}$$

$$V_{1 rms} = \frac{c_1}{\sqrt{2}} = \frac{4v_s}{\sqrt{2}\pi}$$

$$V_{1 rms} = \frac{4v_s}{\sqrt{2}\pi}$$

$$V_{1 rms} = 0.9v_s$$

$$V_{n rms} = \frac{4v_s}{n\sqrt{2}\pi} = \frac{0.9v_s}{n}$$

$$\begin{aligned}
 a_n &= \frac{2}{T} \int_0^T v_o(wt) \cos nwt \cdot dwt \\
 &= \frac{2}{\pi} \int_0^{\pi} v_s \cos nwt \cdot dwt \\
 &= \frac{2v_s}{\pi} [\sin nwt]_0^{\pi}
 \end{aligned}$$

$$a_n = 0$$

$$b_n = \frac{2}{T} \int_0^T v_o(wt) \sin nwt \cdot dwt$$

$$= \frac{2}{\pi} \int_0^{\pi} v_s \sin nwt \cdot dwt$$

$$= \frac{2v_s}{\pi} [-\cos n\pi]_0^{\pi}$$

$$= \frac{2v_s}{\pi} [-\cos n\pi + \cos 0]$$

$$b_n = \frac{2v_s}{\pi} [1 - \cos n\pi] \quad \left\{ \begin{array}{l} \text{for odd values} \\ \text{for even values} \end{array} \right. \quad \left\{ \begin{array}{l} \text{for odd values} \\ \text{for even values} \end{array} \right.$$

$$\therefore b_n = \begin{cases} \frac{4v_s}{\pi} & \text{for odd values} \\ 0 & \text{for even values} \end{cases}$$

Problems:

Q) A single phase FBJ having square wave output has the DC supply of 48V and O/P resistance of $4.8\ \Omega$. Determine rms o/p v_{tg} & $v_{1,\text{rms}}$.

$$\rightarrow v_{0,\text{rms}} = v_s = 48V$$

$$v_{1,\text{rms}} = 0.9 \times v_s = \underline{\underline{43.2V}}$$

Q) A single phase FBJ has resistance load of $2.4\ \Omega$ and the DC input v_{tg} is 48V. Determine rms o/p v_{tg}, o/p power, peak & avg current of each transistor. ($\kappa = 50\%$)

$$\rightarrow v_{0,\text{rms}} = 48V = v_s$$

$$\star \text{ O/P Power} = \frac{v_{0,\text{rms}}^2}{R} = \frac{48^2}{2.4} = \underline{\underline{960W}}$$

$$\star I_T \text{ peak} = \frac{v_s}{R} = \frac{48}{2.4} = \underline{\underline{20A.}}$$

$$\star I_T \text{ avg} = i_T \text{ peak} \times \text{Duty cycle.}$$

$$= 20 \times 0.5$$

$$\boxed{I_T \text{ avg} = 10A}$$


27/01/23


Three phase inverter:

- * Normally used for high power applications.
- * Three phase inverter \leftarrow 180° conduction
 120° conduction
- * The 180° conduction has better utilization of the switches and is the preferred method.

180° degree conduction:

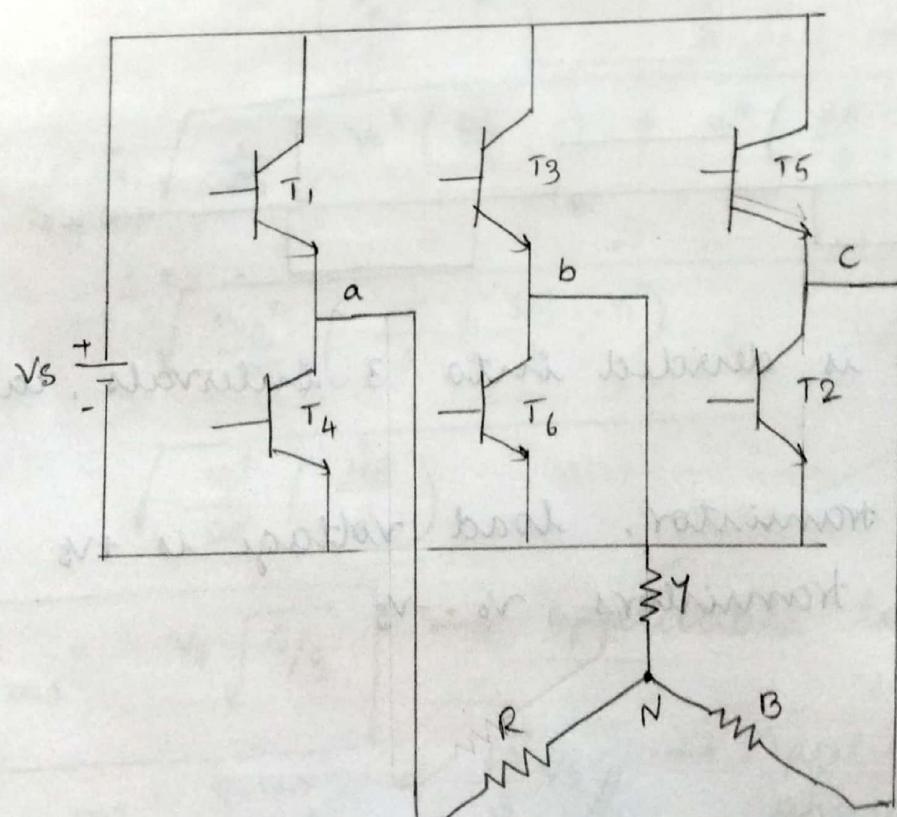- * It consists of 6 transistors (switch)
- * Each transistor conducts for 180° .
- * 3 transistors remain on at a time
- * The resistors R, Y and B connected in star configuration and 'N' is the neutral point.



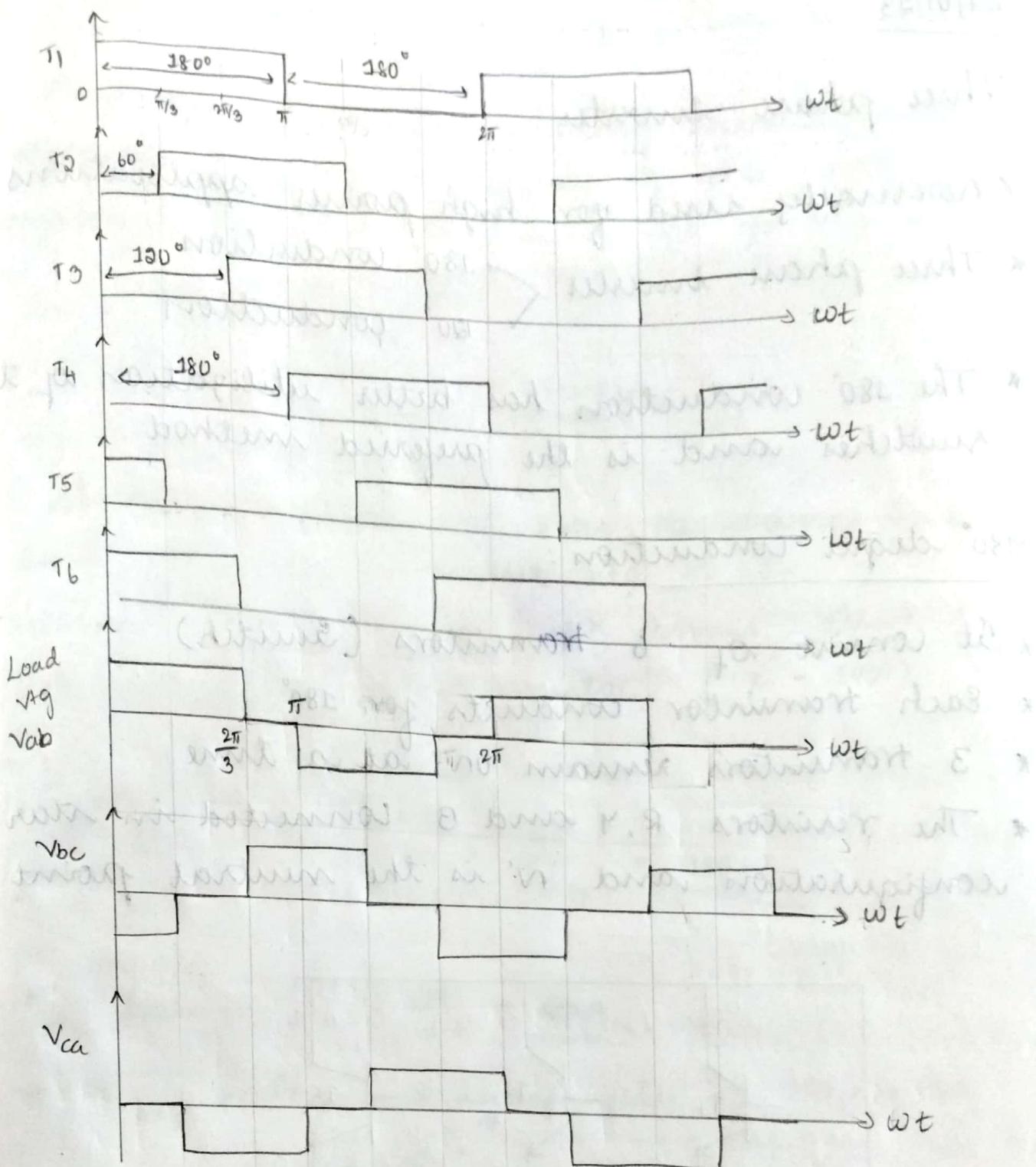

- * Half wave is divided into 3 intervals, each of 60° .
- * For upper transistor, load voltage is $+V_g$
- * For lower transistors $V_o = -V_g$

Interval	conducting transistors	line v _{TG} v _{RY}	Phase v _{TG} , v _{RN}
1	5, 6, 1	v _S	v _S /3
2	6, 1, 2	v _S	2v _S /3
3	1, 2, 3	0	v _S /3
4	2, 3, 4	-v _S	-v _S /3
5	3, 4, 5	-v _S	-2v _S /3
6	4, 5, 6	0	-v _S /3

The line voltage is quasi square wave.
Its rms value is given by

$$\begin{aligned}
 \frac{V_{\text{line } v_{TG}}}{\text{rms}} &= \left[\frac{1}{2\pi} \int_0^{2\pi} v_{RY}^2 dt \right]^{1/2} \\
 &= \sqrt{\frac{1}{2\pi} \left[\int_0^{\pi/3} v_S^2 dt + \int_{\pi}^{5\pi/3} v_S^2 dt \right]} \\
 &= \sqrt{\frac{1}{2\pi} \left[v_S^2 \left(\frac{2\pi}{3} - 0 \right) + v_S^2 \left(\frac{5\pi}{3} - \pi \right) \right]} \\
 &= \sqrt{\frac{v_S^2}{2\pi} \left(\frac{2\pi}{3} + \frac{5\pi}{3} - \pi \right)} \\
 &= \sqrt{\frac{v_S^2}{2\pi} \left(\frac{4\pi}{3} \right)}
 \end{aligned}$$

$$\frac{v_S \sqrt{2}}{\sqrt{3}} = \frac{v_S \sqrt{2}}{3}$$


$$\boxed{V_L \text{ rms} = v_S \sqrt{2/3}} \rightarrow \text{applicable to all 6 line voltage.}$$

$$V_{\text{phase rms}} = \frac{V_L \text{ rms}}{\sqrt{3}} = \frac{\sqrt{2} v_S}{3} \parallel \rightarrow \text{Applicable to all 3 phase v}_{TG}$$

120 degree conduction:

Same circuit and waveform of 180° conduction but half wave is divided into 2 interval of 60° .

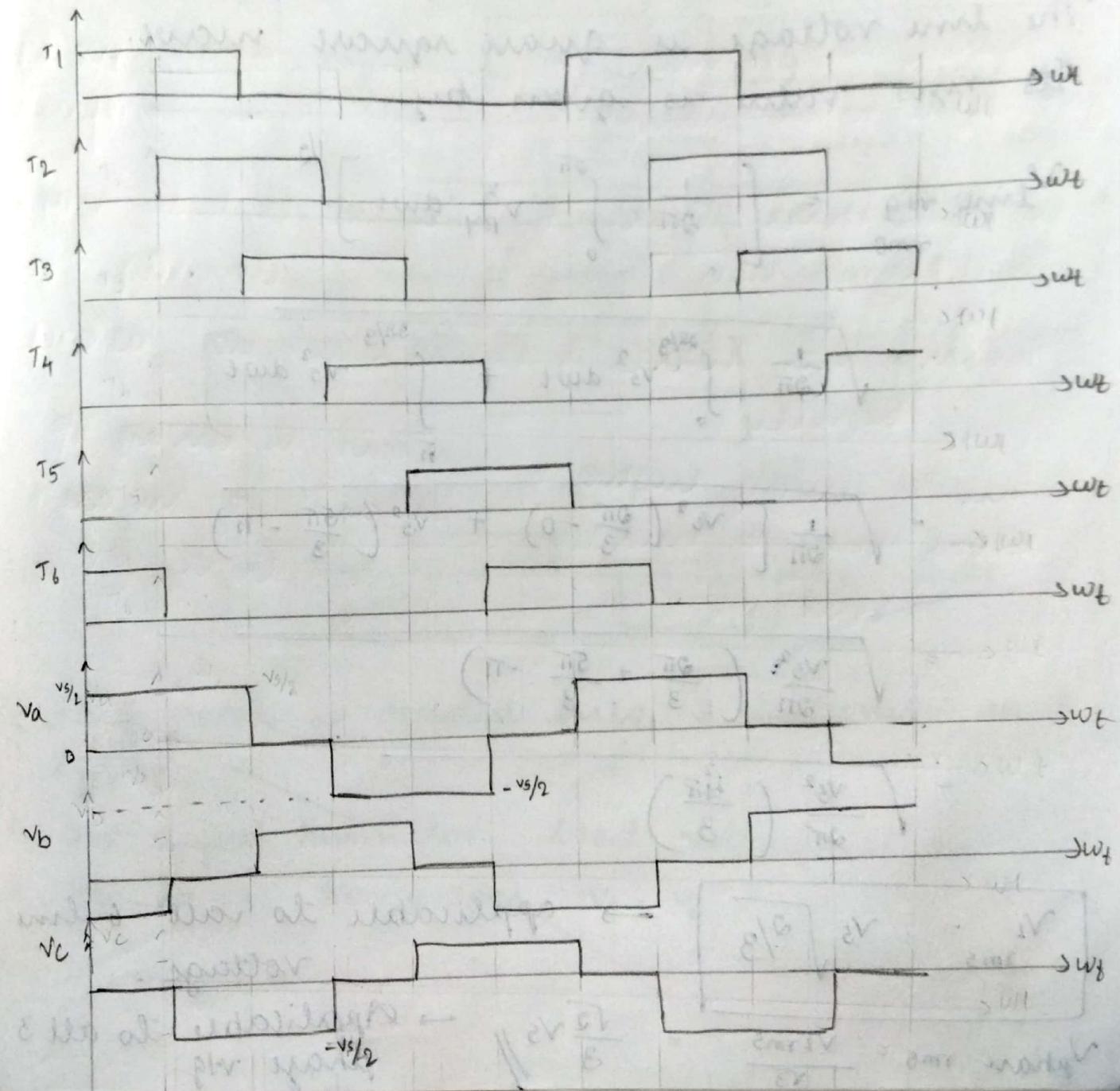- Each transistor conducts for 120° .
- Only two transistors remain on at any instant of time.



Interval	conducting transistors	line vtg $\sqrt{V_s}$	Phase vtg $V_{s/2}$
1	6, 1	$\sqrt{V_s}$	$\sqrt{V_s/2}$
2	1, 2	$\sqrt{V_s/2}$	0
3	2, 3	$-\sqrt{V_s/2}$	$-\sqrt{V_s/2}$
4	3, 4	$-\sqrt{V_s}$	$-\sqrt{V_s/2}$
5	4, 5	$-\sqrt{V_s/2}$	$-\sqrt{V_s/2}$
6	5, 6	$\sqrt{V_s/2}$	0

$$V_{\text{phase rms}} = \sqrt{\frac{1}{2\pi} \left(\int_0^{\frac{2\pi}{3}} \left(\frac{V_s}{2}\right)^2 dt + \int_{\frac{2\pi}{3}}^{\frac{5\pi}{3}} \left(\frac{V_s}{2}\right)^2 dt \right)}$$

$$= \sqrt{\frac{V_s^2}{2\pi} \left[\frac{2\pi}{3} - 0 + \frac{5\pi}{3} - \pi \right]}$$

$$= \sqrt{\frac{V_s^2}{8\pi} \times \frac{4\pi}{3}}$$

$$V_{\text{phase rms}} = \frac{V_s}{\sqrt{6}}$$

$$V_{\text{line vtg}} = \sqrt{3} \times V_{\text{phase rms}}$$

$$= \sqrt{3} \times \frac{V_s}{\sqrt{6}} = \frac{\sqrt{3} \times V_s}{\sqrt{2} \times \sqrt{3}} = \underline{\underline{\frac{V_s}{\sqrt{2}}}}$$


Comparisons between 120° and 180° conduction.

180° conduction

- * Each device conduct for 180°
- * 3 device conducts in one interval
- * Line $v_{tg} \rightarrow$ Quasi square wave with $v_o = \pm v_s$
- * Phase $v_{tg} \rightarrow$ 6 step waveform with $\pm \frac{2v_s}{3}$ & $\pm \frac{v_s}{3}$
- * Cross conduction is possible
- * Devices are better utilized
- * O/P power is higher because of higher v_{tg} level

120° conduction

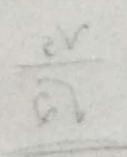- * Each device conduct for 120°
- * 2 device conducts in one interval
- * Line $v_{tg} \rightarrow$ 6 step waveform with $\pm v_s$ & $\pm \frac{v_s}{2}$
- * Phase $v_{tg} \rightarrow$ Quasi square wave with $\pm \frac{v_s}{2}$
- * Cross conduction is not possible.
- * Devices are under utilized.
- * Output power is less because of less lower v_{tg} level.



$$\frac{v}{2} = \frac{v \times 0.5}{2}$$

$$\frac{v}{3} = \frac{v \times 0.33}{3}$$